Single Cycle CPU

Xiufeng Sui

University of Chinese Academy of Sciences (UCAS)





The Processor



- Processor (CPU): Implements the instructions of the Instruction Set Architecture (ISA)
 - Datapath: part of the processor that contains the hardware necessary to perform operations required by the processor ("the brawn")
 - 组合元件和存储元件通过总线或分散方式连接而成的进行数据存储、处理和传送的路径。
 - Control: part of the processor (also in hardware)
 which tells the datapath what needs to be done ("the brain")

Processor Design Process




- Five steps to design a processor:
 - 1. Analyze instruction set → datapath requirements
 - 2. Select set of datapath components & establish clock methodology

Datapath

Control

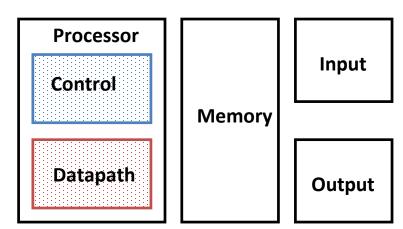 3. Assemble datapath meeting the requirements



- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer
- 5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

The Big Picture: The Performance Perspective



- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- Starting today:
 - Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time
- ET = $IC \times CPI \times Cycle Time$



Processor Datapath and Control




- We're ready to look at an implementation of the MIPS simplified to contain only:
 - memory-reference instructions: lw, sw
 - arithmetic-logical instructions: add, sub, and, or, slt
 - control flow instructions: beq
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - memory-reference? arithmetic? control flow?

MIPS Instruction Formats



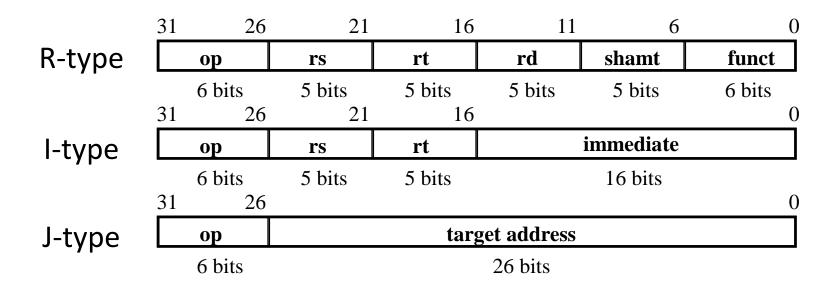- All instructions 32-bits long
- 3 Formats:




The MIPS Subset



- R-Type
 - add rd, rs, rt
 - sub, and, or, slt

31	26	21	16	11	6	0
op	(0)	rs	rt	rd	shamt	funct
6	bits	5 bits	5 bits	5 bits	5 bits	6 bits

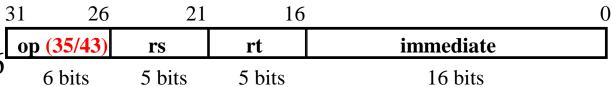- LOAD and STORE
 - lw rt, rs, imm16
 - sw rt, rs, imm16



- BRANCH:
 - beq rs, rt,imm16

0		16	21	31 26	31
	offset	rt	rs	op (4)	
	16 bits	5 bits	5 bits	6 bits	

Basic Steps of Execution



Instruction Fetch

Instruction memory

- Where is the instruction?

address: PC

Decode

– What's the incoming instruction?

- Where are the operands in an instruction? Register file

Execution: ALU

ALU

— What is the function that ALU should perform?

Memory access

Data memory

- Where is my data?

address: effective address

Write back results to registers

Register file


- Where to write?

Determine the next PC


Program counter

Where We're Going: The High-level View



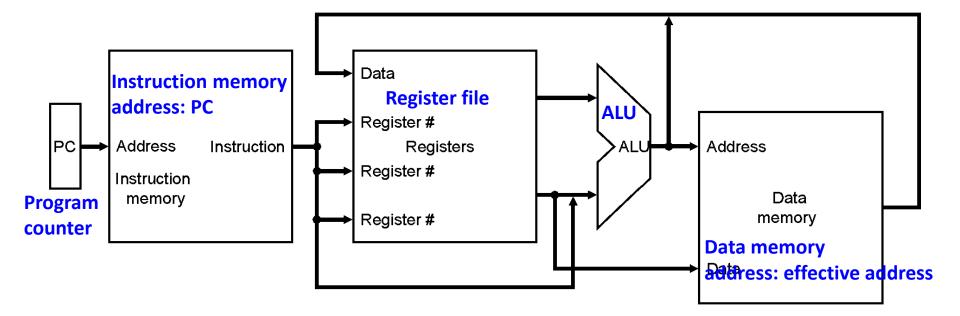


Review: Two Type of Logical Component

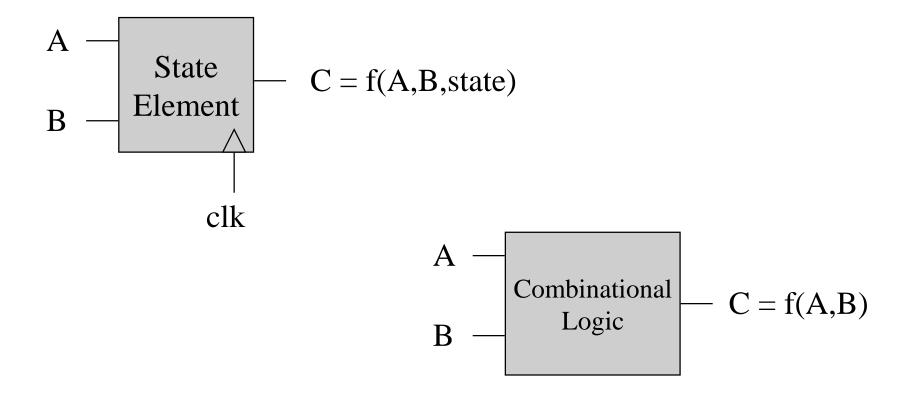


Combinational Elements



- AND-gate
 - Y = A & B

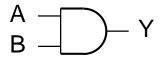


- Multiplexer
 - Y = S ? I1 : I0

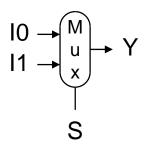


Adder

$$Y = A + B$$

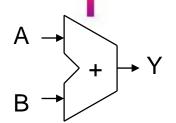


Arithmetic/Logic Unit

$$Y = F(A, B)$$

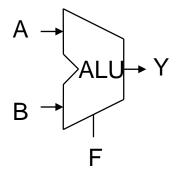


Clocking Methodology (定时方法)



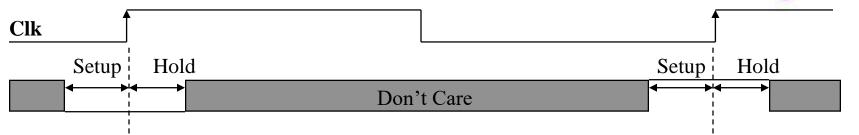

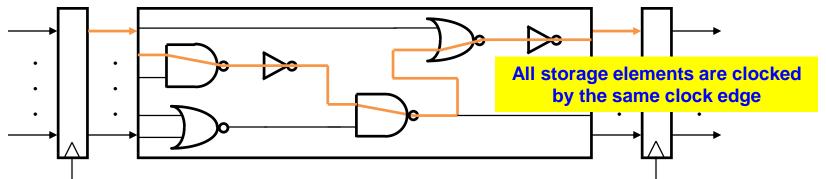- Setup Time: how long the input must be stable before the CLK trigger for proper input read
- Hold Time: how long the input must be stable after the CLK trigger for proper input read
- CLK-to-Q Delay: how long it takes the output to change, measured from the CLK trigger




- The critical path is the longest delay between any two registers in a circuit
- Critical path determines length of clock period
 - The clock period must be longer than this critical path, or the signal will not propagate properly to that next register
 - This includes CLK-to-Q delay and setup delay

Storage Element: The Register



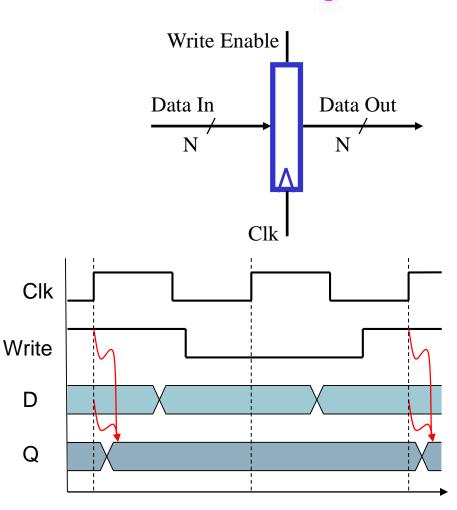
- Register
 - Similar to the D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - 0: Data Out will not change
 - 1: Data Out will becomeData In (on the clock edge)
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later



Storage Element: Register File



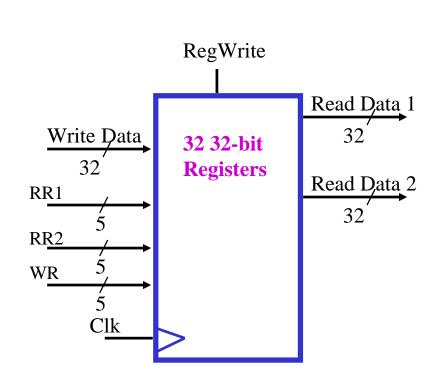
- Register File consists of (32) registers:
 - Two 32-bit output buses
 - One 32-bit input bus
- Register is selected by:
 - RR1 selects the register to put on bus "Read Data 1"
 - RR2 selects the register to put on bus "Read Data 2"
 - WR selects the register to be written
 - via WriteData when RegWrite is
- Clock input (CLK)



Inside the Register File



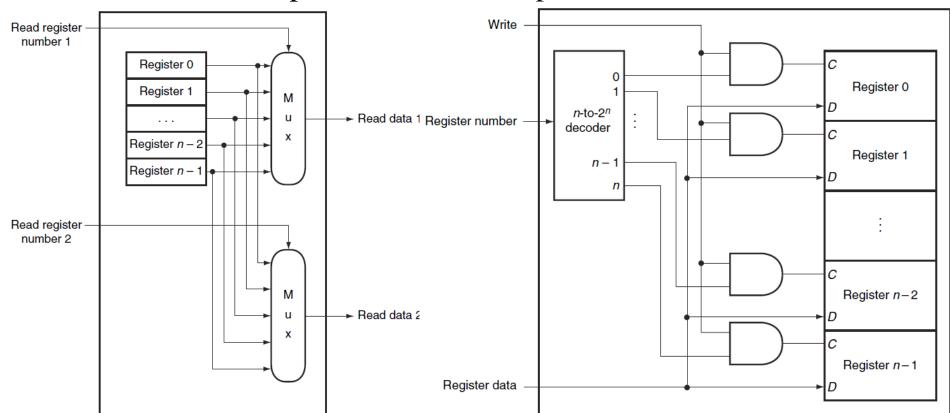
- The implementation of two read ports register file
 - n registers
 - done with a pair of n-to-1 multiplexors, each 32 bits wide.



Storage Element: Memory



- Memory
 - Two input buses: WriteData, Address
 - One output bus: ReadData
- Memory word is selected by:
 - Address selects the word to put on ReadData bus
 - If MemWrite = 1: address selects the memory word to be written via the WriteData bus
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => ReadData valid after "access time."

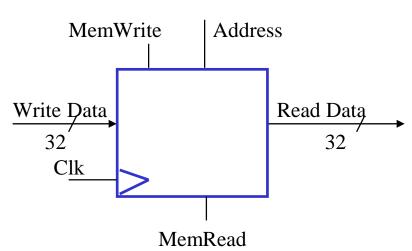

RTL: Register Transfer Language



- Describes the movement and manipulation of data between storage elements:
 - R[i]表示寄存器堆中寄存器i的内容
 - M[addr]表示存储单元addr的内容
 - 传送方向用<- 表示, 传送源在右目的在左
 - 程序计数器PC直接用PC表示其内容


```
R[3] <- R[5] + R[7]

PC <- PC + 4 + R[5]

R[rd] <- R[rs] + R[rt]

R[rt] <- Mem[R[rs] + immed]
```

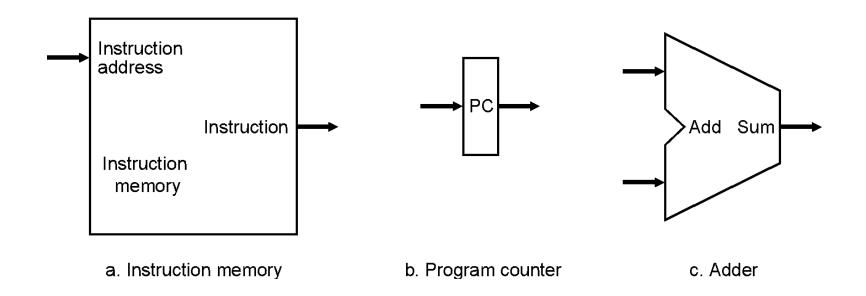
Instruction Fetch and Program Counter Management



Overview of the Instruction Fetch L


INSTITUTE OF COMPUTING TECHNOLOGY

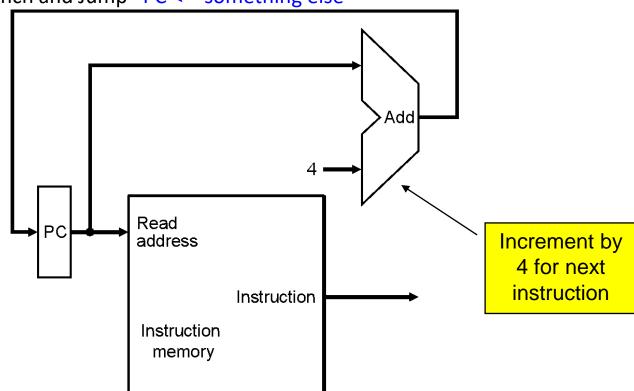- The common RTL operations
 - Fetch the Instruction: inst <- mem[PC]</p>
 - Update the program counter:
 - Sequential Code: PC <- PC + 4
 - Branch and Jump PC <- "something else"



Datapath for Register-Register Operation

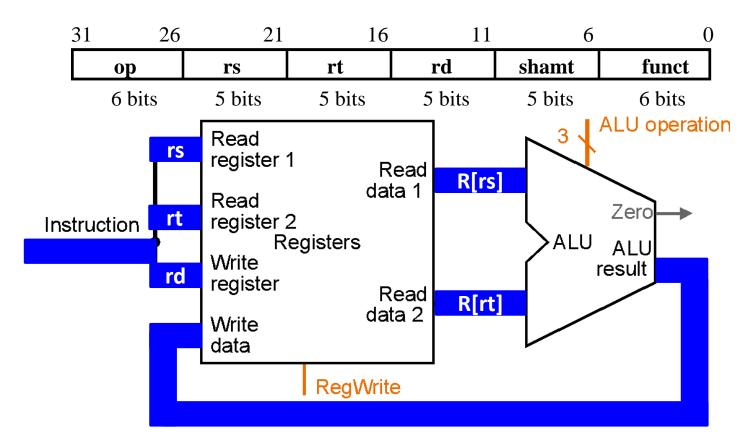
- R[rd] <- R[rs] op R[rt] Example: add rd, rs, rt
 - RR1, RR2, and WR comes from instruction's rs, rt, and rd fields
 - ALUoperation and RegWrite: control logic after decoding instruction



Datapath for Load Operations

中斜柱计算符 INSTITUTE OF COMPUTING TECHNOLOGY

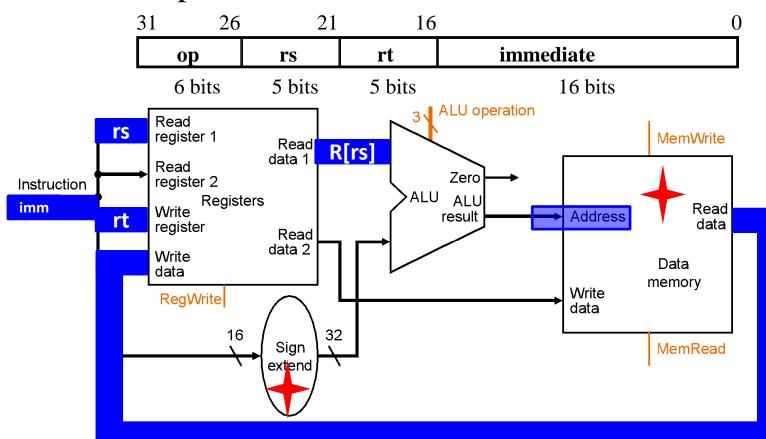
- R[rt] <- Mem[R[rs] + SignExt[imm16]]
 - Example: *lw* rt, rs, imm16







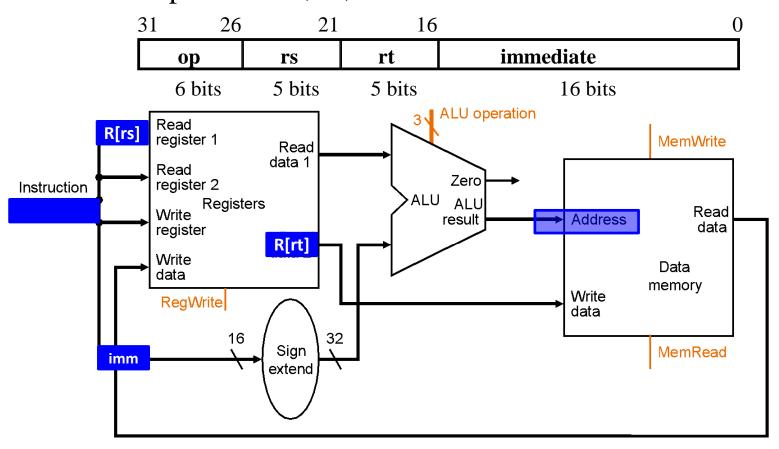- Mem[R[rs] + SignExt[imm16]] <- R[rt]
 - Example: sw rt, rs, imm16



Datapath for Branch Operations




- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - Already calculated by instruction fetch

Datapath for Branch Operations



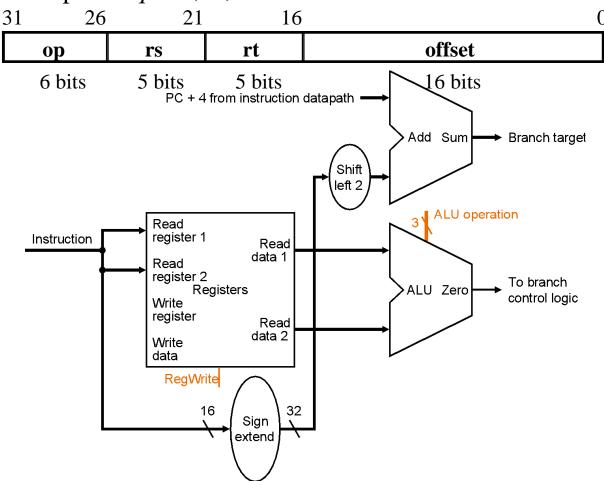
- Z <- (rs == rt); if Z, PC = PC+4+imm16; else PC = PC+4
 - Example: beq rs, rt, imm16



Datapath for Branch Operations



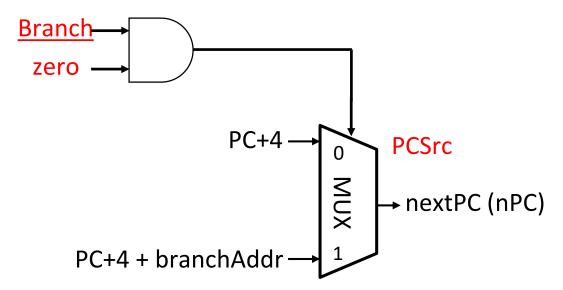- Revisit "next address logic":
 - PCSrc should be 1 if branch, 0 otherwise



Branch	zero	PCSrc
0	0	0
0	1	0
1	0	0
1	1	1

How does this change if we add bne?

Binary Arithmetic for the Next Address




- In theory, the PC is a 32-bit byte address into the instruction memory:
 - Sequential operation: PC < 31:0 > = PC < 31:0 > +4
 - Branch operation: PC<31:0> = PC<31:0> + 4 + SignExt[Imm16] * 4
- The magic number "4" always comes up because:
 - The 32-bit PC is a byte address
 - And all our instructions are 4 bytes (32 bits) long
 - The 2 LSBs (Least Significant Bit) of the 32-bit PC are always zeros
 - There is no reason to have hardware to keep the 2 LSBs
- In practice, we can simplify the hardware by using a 30-bit PC<31:2>:
 - Sequential operation: PC<31:2> = PC<31:2> + 1
 - Branch operation: PC<31:2> = PC<31:2> + 1 + SignExt[Imm16]
 - In either case: Instruction Memory Address = PC<31:2> concat "00"

Putting it All Together: A Single Cycle Datapath



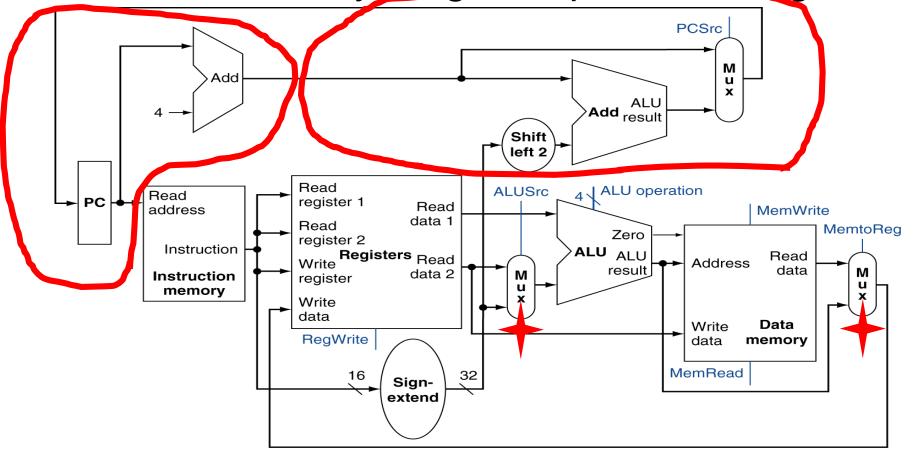We have everything except control signals




Key Points



- CPU is just a collection of state and combinational logic
- We just designed a very rich processor, at least in terms of functionality
- ET = $IC \times CPI \times Cycle Time$
 - where does the single-cycle machine fit in?

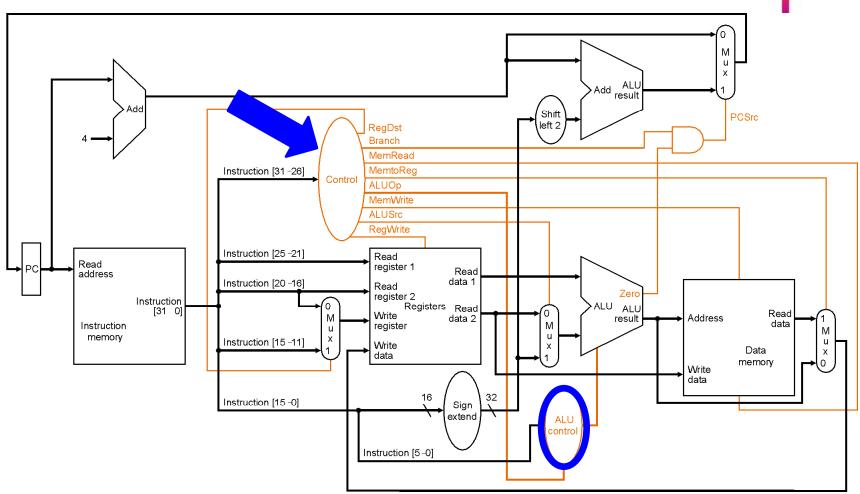Okay, then, what about those Control Signals?






ALU control bits

中斜代计算码 INSTITUTE OF COMPUTING TECHNOLOGY

• 5-Function ALU

ALU control input	Function	Operations
000	And	and
001	Or	or
010	Add	add, lw, sw
110	Subtract	sub, beq
111	Slt	slt

Full ALU

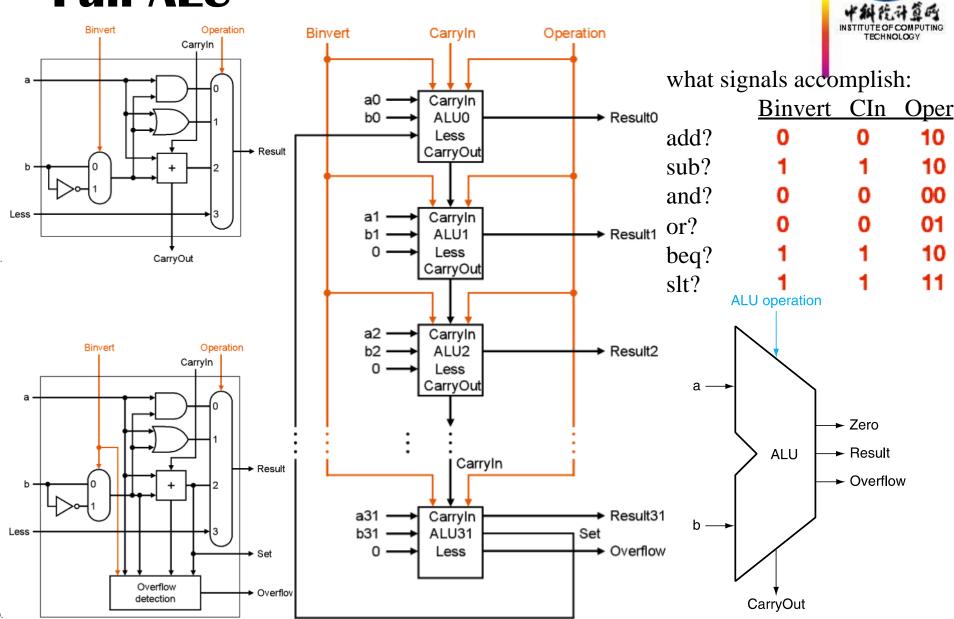

ALU control bits



5-Function ALU

ALU control input	Function	Operations
000	And	and
001	Or	or
010	Add	add, lw, sw
110	Subtract	sub, beq
111	Slt	slt


- based on opcode (bits 31-26) and function code (bits 5-0) from instruction
- ALU doesn't need to know all opcodes--we will summarize opcode with ALUOp (2 bits):
 - 00 lw,sw 01 beq 10 R-format



Generating ALU Control



Instruction opcode	ALUOp	Instruction operation	Function code	Desired ALU action	ALU control input
lw	00	load word	XXXXXX	add	010
SW	00	store word	XXXXXX	add	010
beq	01	branch eq	XXXXXX	subtract	110
R-type	10	add	100000	add	010
R-type	10	subtract	100010	subtract	110
R-type	10	AND	100100	and	000
R-type	10	OR	100101	or	001
R-type	10	slt	101010	slt	111

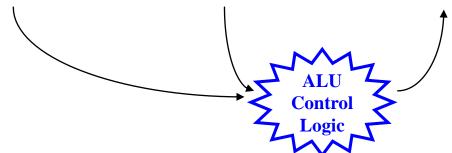

The Main Control Unit




Control signals derived from instruction

R-type	0	rs	rt	l	rd	shamt	t	funct
	31:26	25:21	20:16	15	5:11	10:6		5:0
Load/	35 or 43	rs	rt			addre	SS	
Store				-				
	31:26	25:21	20:16 1	\		15:C)	
Branch	4	rs	rt		address			
	31:26	25:21	20:16			15:0		
				/	<u> </u>			
	opcode	always	read,		write	for	,	sign-extend
		read	except		R-ty	/pe		and add
	'		for load		and I	oad		

Controlling the CPU



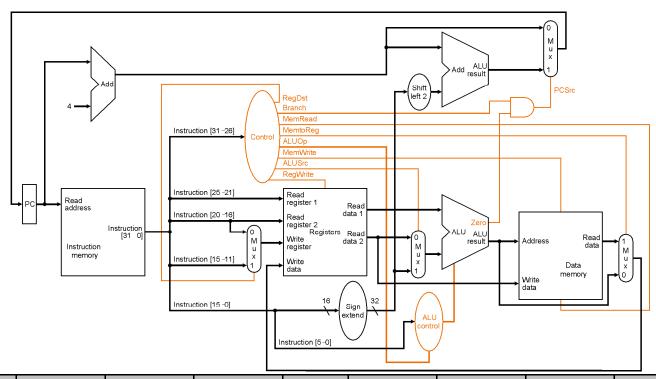

Instruction	RegDst	ALUSrc	Memto- Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
SW	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Control Truth Table





		R-format	lw	SW	beq
Opcode		000000	100011	101011	000100
	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
Outputs	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

Control



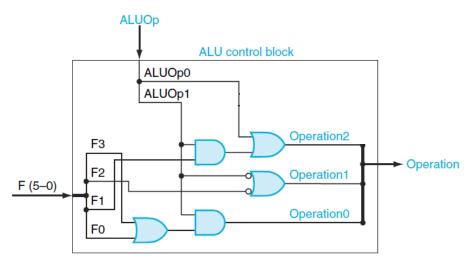
Simple combinational logic (truth tables)



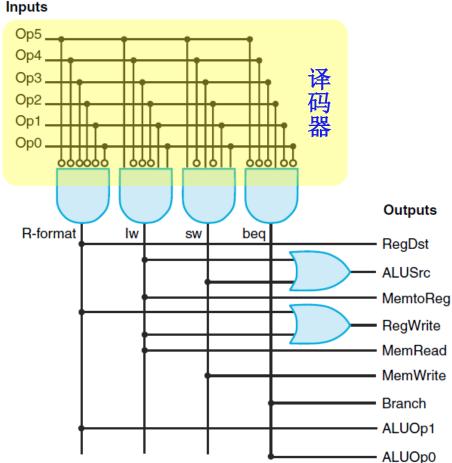


Datapath With Control



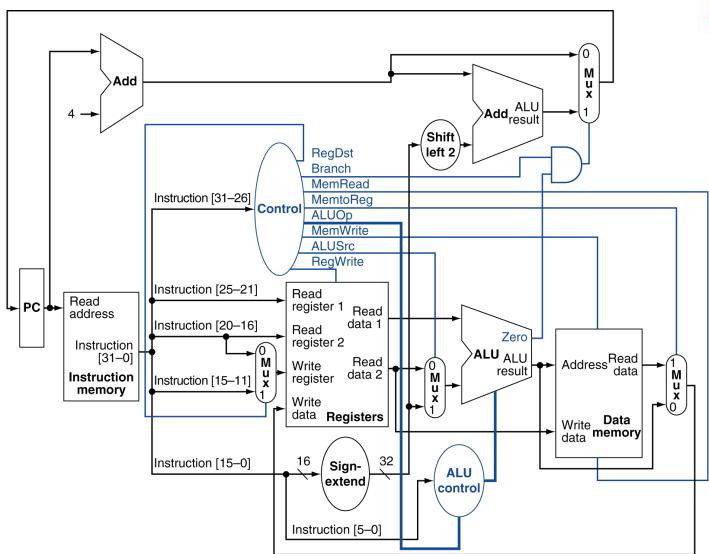


R-Type Instruction



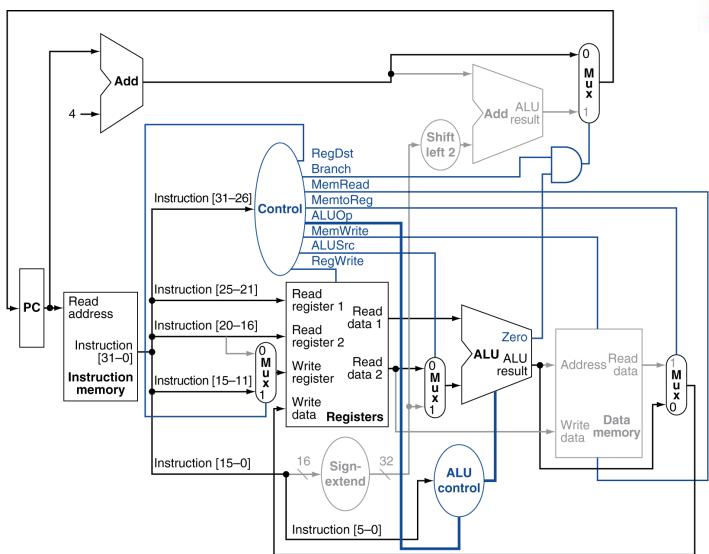


Load Instruction



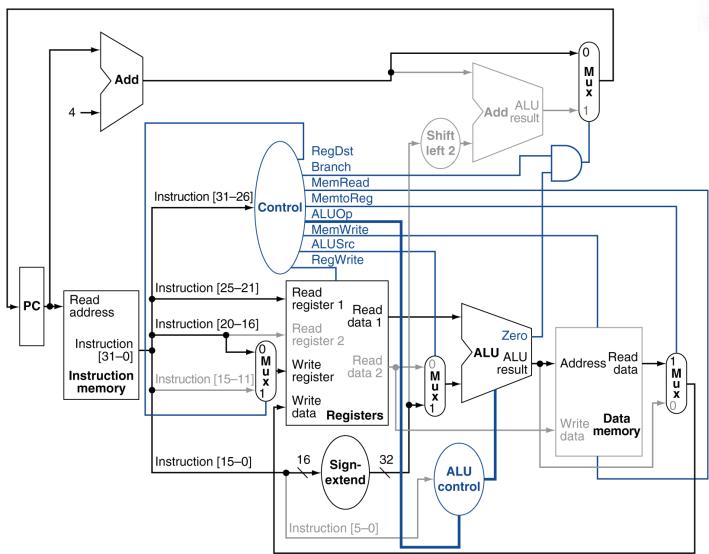

Branch-on-Equal Instruction



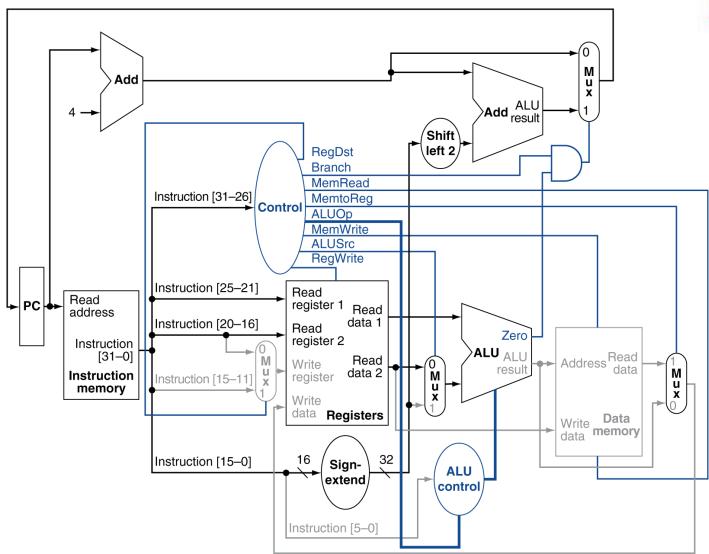

Implementing Jumps




- Jump uses word address
- Update PC with concatenation of
 - Top 4 bits of (PC+4)
 - 26-bit jump address
 - -00
- Need an extra control signal decoded from opcode


Jump	2	address
	 31·26	25:0

Datapath With Jumps Added



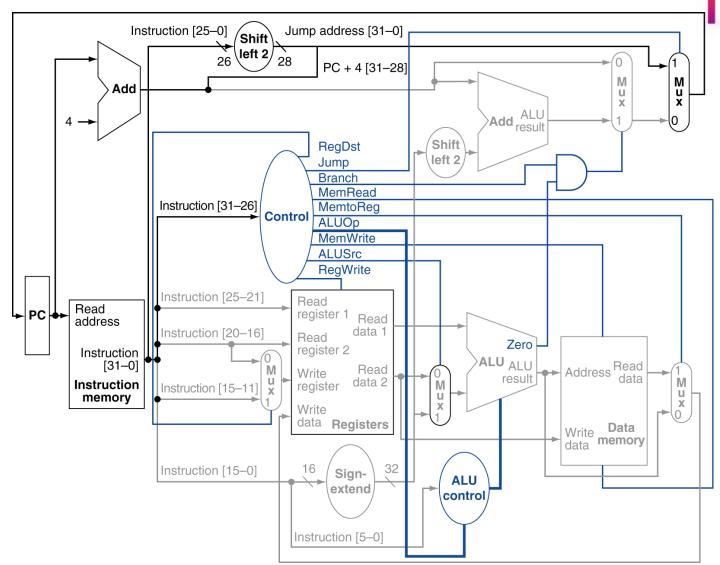


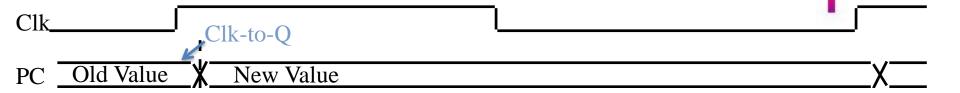Register-Register Timing: One Complete Cycle for add






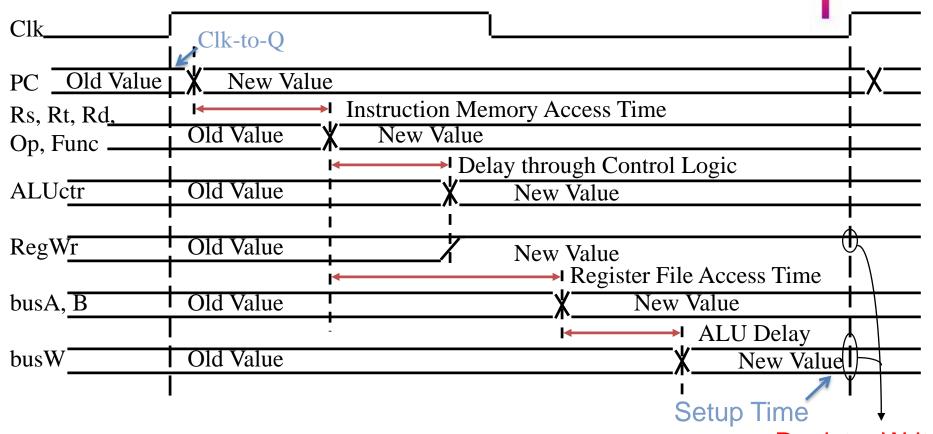Register-Register Timing: One Complete Cycle for add



Register Write
Occurs Here

W指令的执行时间最长,它所花时间作为财产的周期

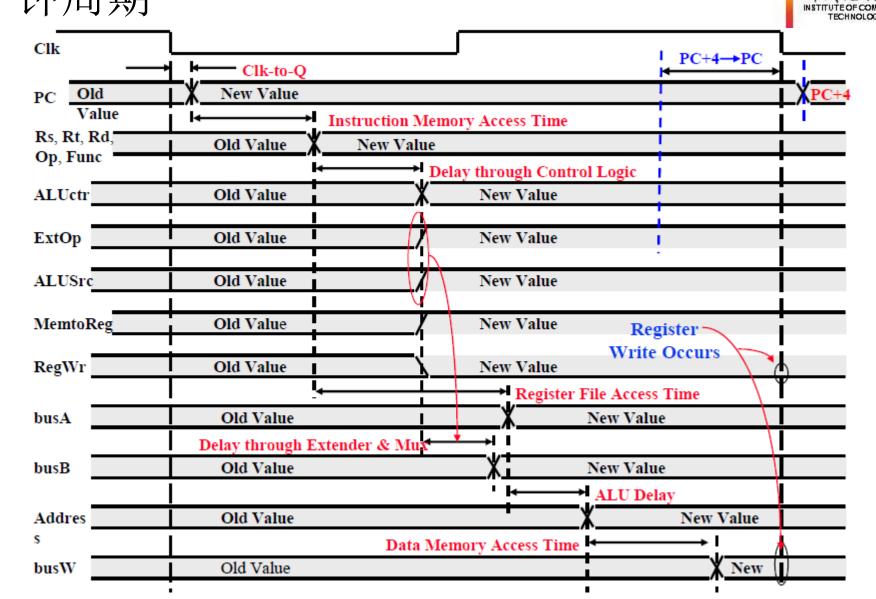

单周期数据通路的性能



- 假设在该实现方式中,主要功能单元的操作时间如下:
 - 存储单元: 200 ps
 - ALU和加法器: 100 ps
 - 寄存器堆(读或写): 50 ps
- 假设其他部件没有延迟,下面方法中哪个更快?快多少?
 - 每条指令在一个固定长度的时钟周期内完成;
 - 每条指令在一个可变长度的时钟周期内完成,时钟周期长度仅为指令所需。
 - 为比较性能,假设指令的组成比例为25% loads, 10% stores, 45% ALU instructions, 15% branches, and 5% jumps。

Single-Cycle CPU Summary



- Easy, particularly the control
- Which instruction takes the longest? By how much?
 Why is that a problem?
 - ET = IC \times CPI \times CT
- What else can we do?
- When does a multi-cycle implementation make sense?
 - e.g., 70% of instructions take 75 ns, 30% take 200 ns?
 - suppose 20% overhead for extra latches
- Real machines have much more variable instruction latencies than this.