

# Arithmetic Logic Unit


Xiufeng Sui

University of Chinese Academy of Sciences (UCAS)




中国科学院  
INSTITUTE OF COMPUTING TECHNOLOGY
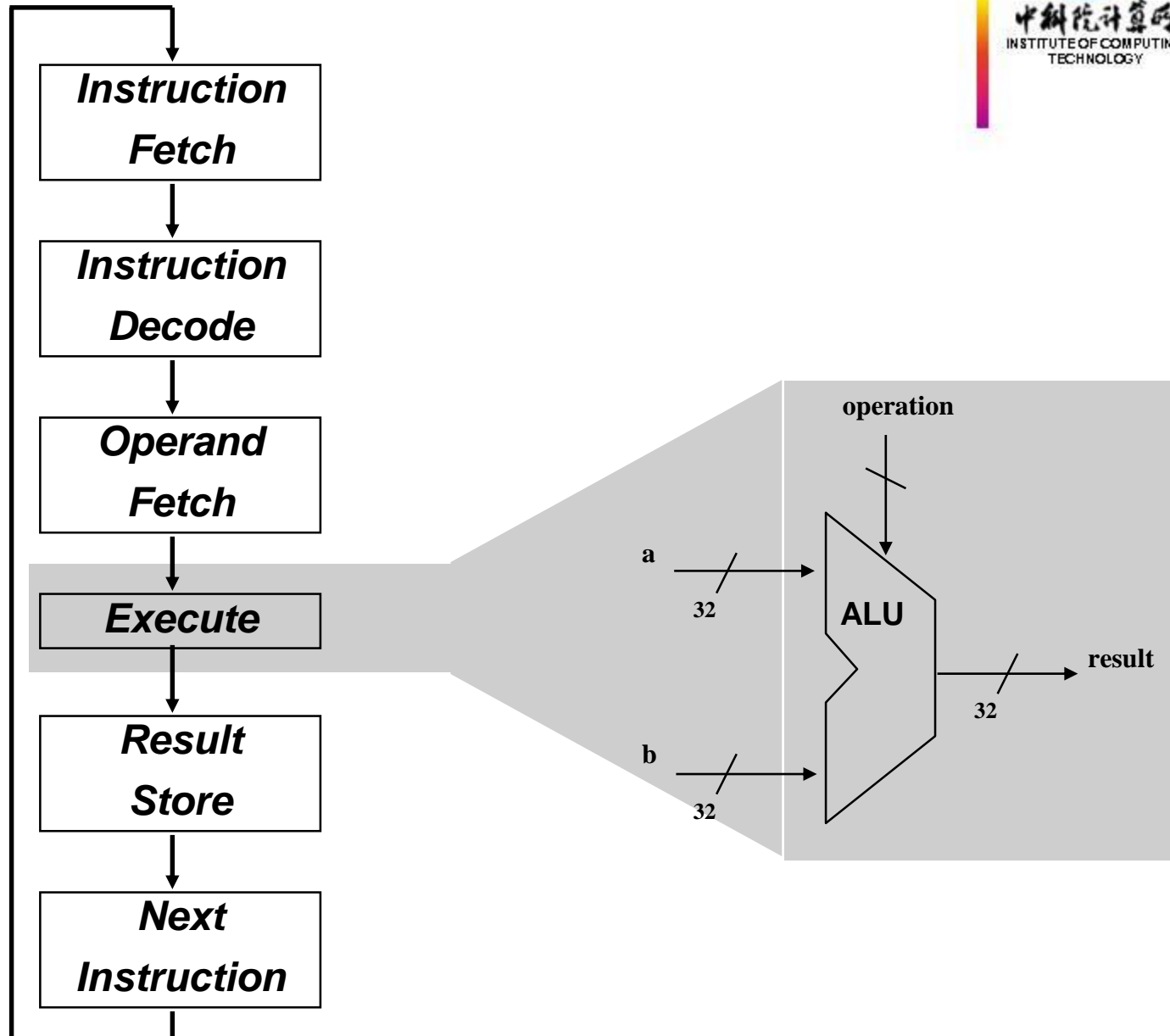
# Arithmetic -- The heart of instruction execution





# Designing an Arithmetic Logic Unit

 

ALU control input	Function	Operations
000	And	and
001	Or	or
010	Add	add, lw, sw
110	Subtract	sub, beq
111	Slt	slt

  
# A One Bit ALU

- This 1-bit ALU will perform AND, OR, and ADD




# A 32-bit ALU

## 1-bit ALU

 


## 32-bit ALU

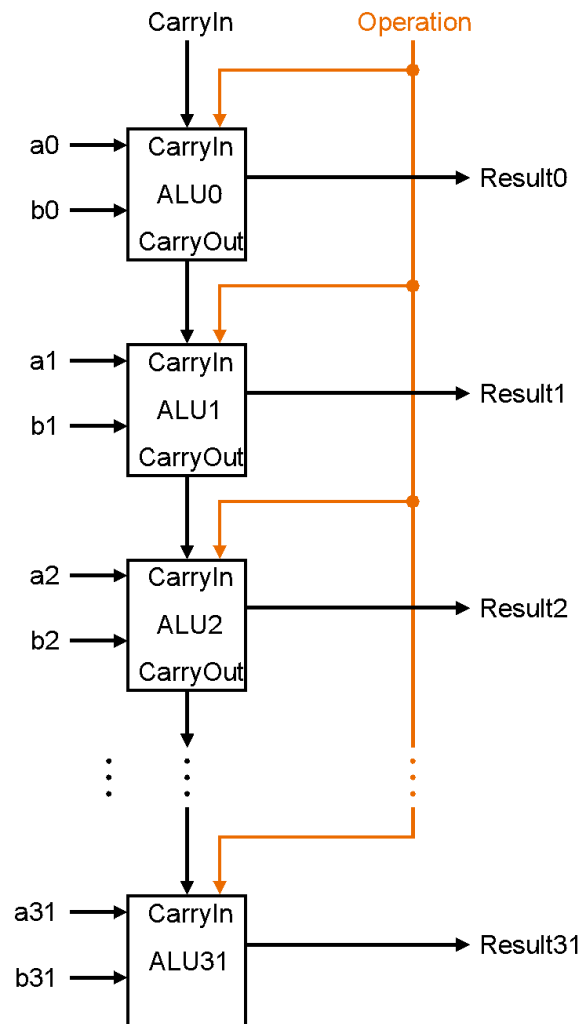

$$\begin{array}{rcccc}
 & 1 & 0 & 0 & 0 \\
 & \swarrow & \swarrow & \swarrow & \swarrow \\
 + & 1 & 1 & 0 & 1 \\
 \hline
 & 0 & 1 & 1 & 1
 \end{array}$$
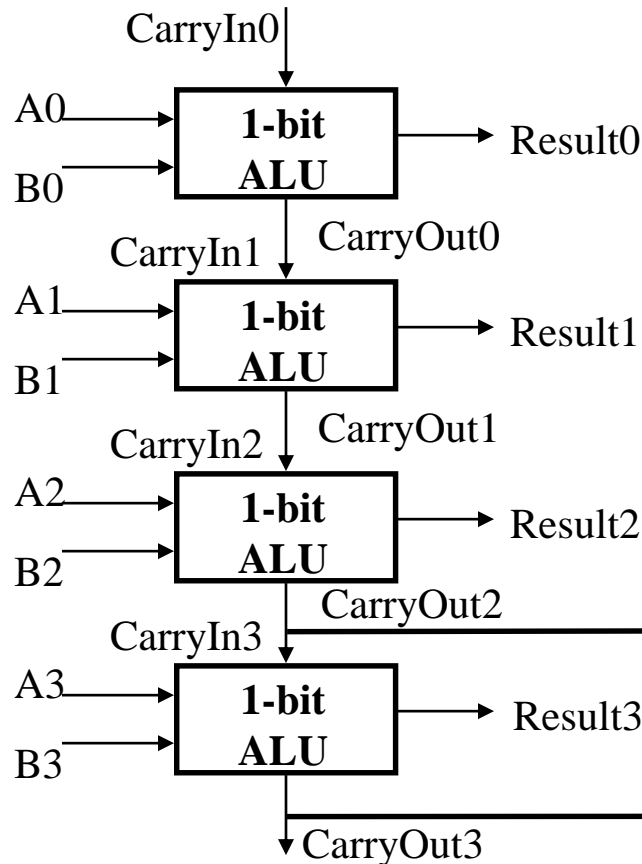
# Overflow Detection Logic

- Carry into MSB  $\neq$  Carry out of MSB
  - For a N-bit ALU:  $\text{Overflow} = \text{CarryIn}[N - 1] \text{ XOR } \text{CarryOut}[N - 1]$




X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

**Overflow**
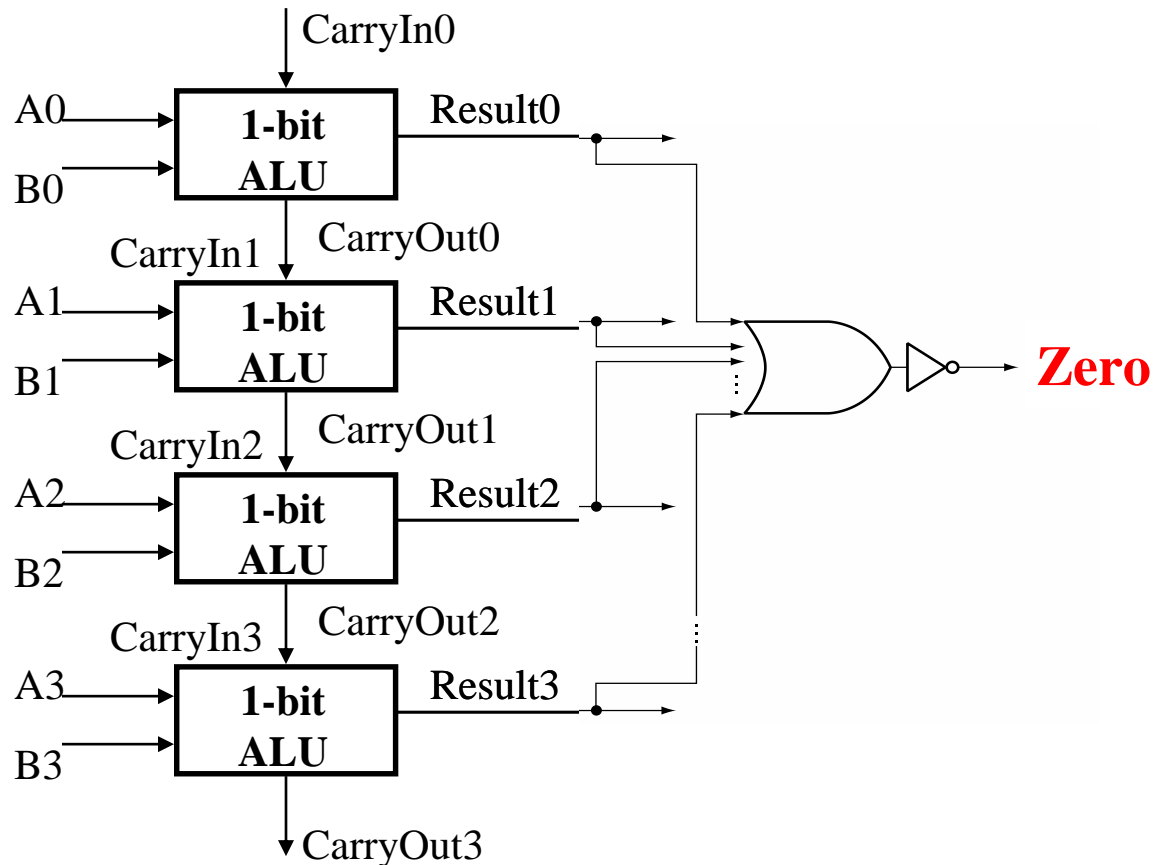
# Zero Detection Logic

- Zero Detection Logic is just one BIG NOR gate
  - Any non-zero input to the NOR gate will cause its output to be zero








# Set-on-less-than

- We are mostly there!
  - $A < B \Rightarrow (A - B) < 0$
  - Do a subtract
- If true, set LSB to 1, all others 0
  - Use sign bit
    - route to bit 0 of result
    - all other bits zero
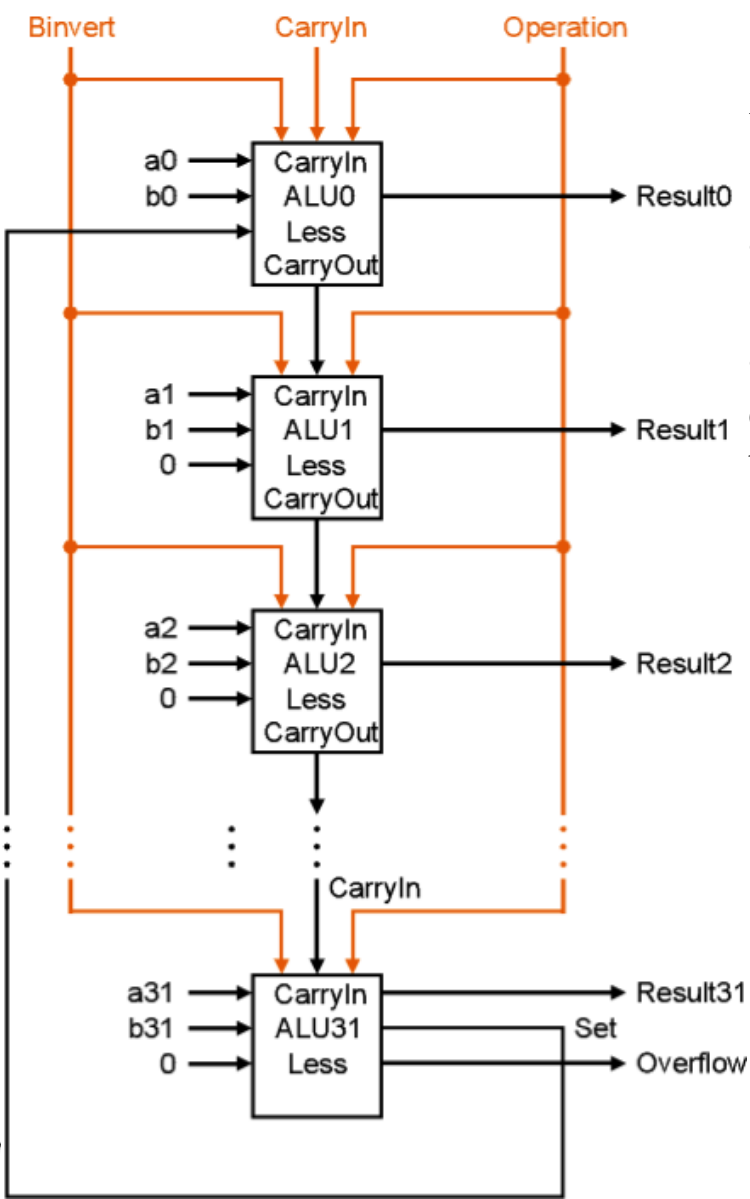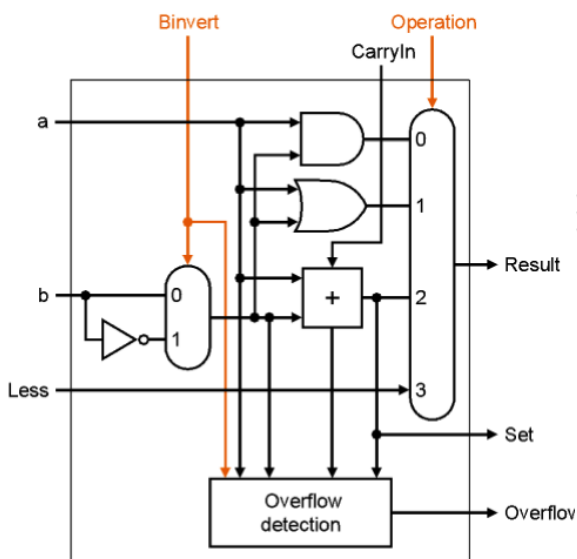 
# Full ALU




中科院计算所  
INSTITUTE OF COMPUTING  
TECHNOLOGY



what signals accomplish:



	Binvert	CIn	Oper
add?	0	0	10
sub?	1	1	10
and?	0	0	00
or?	0	0	01
beq?	1	1	10
slt?	1	1	11

ALU operation

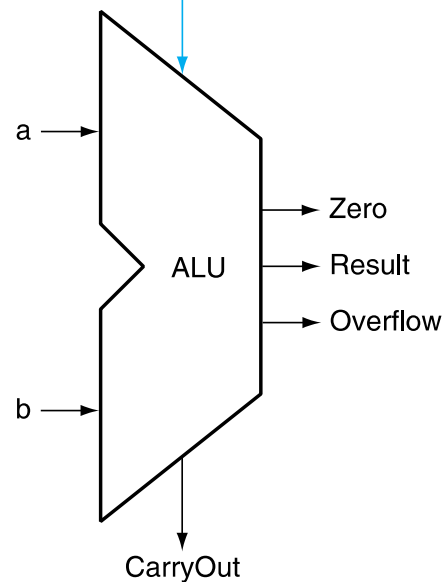
 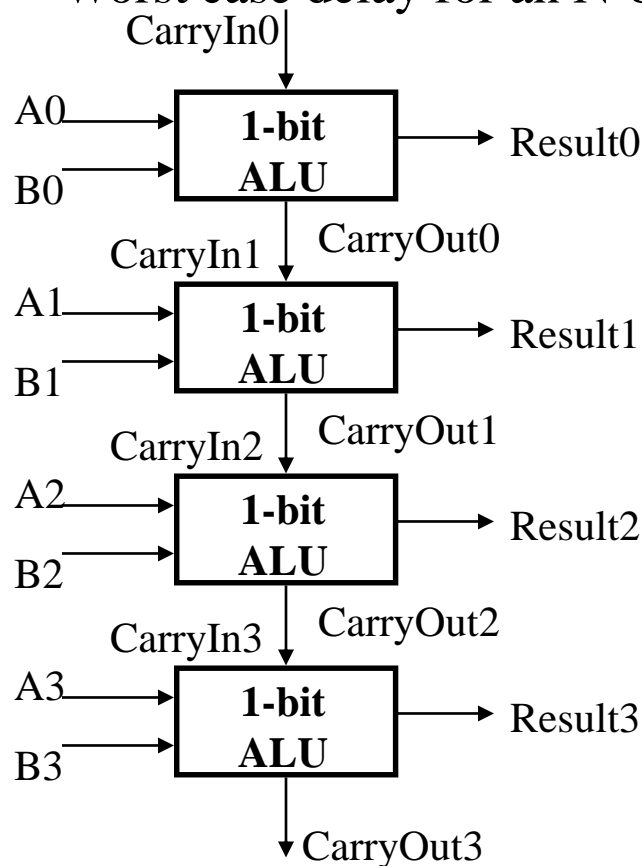
# The Disadvantage of Ripple Carry

- The adder we just built is called a “Ripple Carry Adder”
  - The carry bit may have to propagate from LSB to MSB
  - Worst case delay for an N-bit RC adder:  $2N$ -gate delay



The point -> ripple carry adders are slow. Faster addition schemes are possible that *accelerate* the movement of the carry from one end to the other.